

Electricity



TRY YOURSELF

ANSWERS


- The physical quantity coulomb/second is called electric current.
- Conventional current in the direction of flow of positive charge.
- (b)** : As we know that, work done, $W = qV = 0.5 \times 20 = 10 \text{ J}$
- (b)** : Work done in moving an unit charge across two points in an electric circuit is a measure of potential difference.
- S.I. unit of potential difference is volt.
- (b)** : If area of cross-section is halved, then, resistance becomes,

$$R' = \rho \frac{l}{A'} = \rho \frac{l}{A/2} = \frac{2\rho l}{A} = 2R$$

(Taking length remains in changed)

So, the resistance increases two times of its original.
- Resistance of a pure metal increases with rise in temperature.
- S.I. unit of resistivity is ohm-meter ($\Omega\text{-m}$).

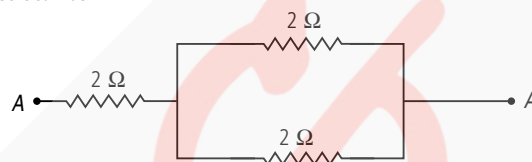- By combining two resistors each of 2Ω in parallel and then their equivalent with other 2Ω resistor we can obtain 3Ω resistance.



$$\frac{1}{R_1} = \frac{1}{2} + \frac{1}{2} = 1 \Omega \text{ and } R_{eq.} = 2 + 1 = 3 \Omega$$

- (b)** : In homes electrical devices are connected in parallel.
- (b)** : If the potential difference across each resistor is same then the resistors are connected in parallel.
- (b)** : If a current of 3.5 A flows through a hair dryer, then for normal use of fuse with rating 5 A will be most suitable among given options.
- Given, power of the lamp, $P = 25 \text{ W}$ and voltage, $V = 200 \text{ V}$.
 \therefore Power, $P = VI$
 $\Rightarrow I = \frac{P}{V} = \frac{25 \text{ W}}{200 \text{ V}} = \frac{1}{8} \text{ A} = 0.125 \text{ A}$

